

Section I [Individual Work]

1) True-False

Print True (T) or False (F), whichever is *more appropriate*, following each statement. Please include in your answer why you believe the answer is true or false. Please be succinct.

- (a) During the discharge of an output node (in a logic gate) the energy stored in its capacitance is dumped into ground.

T:

- (b) Logical effort g is independent of the size of the transistors in a logic gate.

T: logical effort is related to gate ratios and topology.

- (c) Gate leakage of PMOS transistors is lower than NMOS transistors of the same t_{ox} .

T: electron mobility > hole mobility

- (d) The larger the transistors in the critical path of a circuit, the lower the delay.

F:

$\tau = RC$ Large transistors increase R which increase τ .

- (e) The dynamic power dissipation of a NAND gate whose one input is grounded, equals zero.

0! $\Rightarrow D = V_0 f$: If other input has frequency f between logic 0 or 1,

$P_{dynamic} = \alpha C V^2 f$ $P_{dynamic}$ is non-zero.

- (f) Method of Logical Effort is used to optimize the power dissipation in a digital CMOS circuit.

F: Method of Logical Effort is used to minimize delay or latency in a CMOS circuit.

- (g) High V_t transistors can be used in non-critical paths to save energy.

T: High V_t is used in non-critical path

Low V_t is used in critical path

- (h) Instantaneous power is used to determine the wire thickness.

T:

$P = IV = \frac{V^2}{R}$ wire thickness $\propto \frac{1}{R}$

- (i) A digital circuit sized for minimum delay, has the maximum power consumption.

F:


$P = \alpha C V^2 f$

V_{DD}

Power consumption is most affected by V_{DD} .

- (j) The ratio of the stored energy at the output capacitance of an inverter to the heat dissipated by its PMOS transistor is 1.

T:

 

2) Multiple Choice Questions

Print the letter corresponding to the *most appropriate* answer and add an explanation as to why that is the best answer.

- (a) If the optimum number of inverters driving a load is 5, and the input capacitance of the first inverter is 3 units, what is the input capacitance of the last inverter?

(b) 15

☒ (b) 768

(c) 48

(d) 1875



$$N = \log_4 (F) = 5$$

$$F = 1024$$

$$4^4 \cdot 3 = 768$$

- 3) If we ignore the parasitic delay of inverters, the optimum stage effort is

(a) 4.

(b) π .

☒ (c) e.

(d) 2.

- 4) Short-circuit power dissipation is typically about of the total dynamic power?

☒ (a) 10%

(b) 30%

(c) 50%

(d) 70%

Relates to transistor switch, both PMOS/NMOS can be on at the same time

5) Decreasing which parameter among the following is most effective in reducing dynamic power dissipation?

- (a) Frequency
- (b) Switching activity
- (c) Power supply voltage
- (d) Effective capacitance

$$P_{\text{dynamic}} = \alpha C V_{DD}^2 f$$

6) If all transistor sizes are the same, and if all inputs are low (i.e. 0), which of the following logic gates has the highest static energy dissipation?




- (a) Inverter
- (b) NAND
- (c) NOR
- (d) Tristate inverter

3) Logical Effort

For the conventional CMOS logic gate implementing $Z = (A + BC)(E + \bar{F})$ find p and g for different inputs.


$$Z = (A + BC)(E + \bar{F}) \quad \text{NOR}$$
   
$$Z = [A \text{ NOR } [B \text{ NOR } C]] \text{ NOR } [E \text{ NOR } F]$$



 4) Delay Optimization

Consider the following circuit. The input NAND has an input capacitance of 10 units. The output capacitance is equivalent to 85 units. The units can be considered W/L of a transistor with minimum width and length. Assume that the polarity of the output is not important.



A) Beside each logic gate indicate p , g , b , and h .

$$C_{in} = \frac{5}{3} \cdot 1 \cdot 37.83 / 6.32 = 10$$

$$C_{in} = \frac{5}{3} \cdot 2 \cdot 71.73 / 6.32 = 37.83$$

$$C_{in} = \frac{4}{3} \cdot 4 \cdot 85 / 6.32 = 71.73$$

$$C_{in} = g b C_{out} / f_{min}$$

B) Calculate the path effort F for the critical path in the circuit.

$$F = B G H$$

$$H = 85/10 = 8.5$$

$$G = \frac{5}{3} \cdot \frac{5}{3} \cdot \frac{4}{3} = \frac{100}{27}$$

$$B = 1 \cdot 2 \cdot 4 = 8$$

$$F = B G H = 8 \cdot \frac{100}{27} \cdot 8.5 = 251.85$$

$$251.85^{1/3} = 6.32 f_{min}$$

C) Find the optimum number of stages \hat{N} for minimizing the delay in the circuit. Modify the circuit, if necessary to achieve the minimum delay. Revise the parameters p , g , b , and h for the logic gates and include inserted inverters.

$$\hat{N} = \log_4 F = \log_4 (251.85) = 4$$

$$F = \pi B G H = (2 \cdot 4) \left(\frac{7}{3} \cdot \frac{4}{3} \cdot \frac{5}{3} \right) (8.5)$$

$$= 352.60^{1/4} = 4.33$$

W	p=1	x	p=3	y	p=2	z	p=2
	g=1		g=7/3		g=4/3		g=5/3
	b=1		b=1		b=2		b=4
	h=4.34		h=1.85		h=1.62		h=.65

D) Calculate the minimum possible *normalized* and *absolute* delays for the circuit.

Normalized: $1 \cdot \frac{7}{3} \cdot \frac{4}{3} \cdot \frac{5}{3}$

Absolute: $1 \cdot 7 \cdot 4 \cdot 5$

E) Find the unknown input capacitances for the logic gates, including any inserted inverters.


$$C_{inW} = 1 \cdot 1 \cdot 43.43 / 4.33 = 10$$

$$C_{inX} = \frac{7}{3} \cdot 1 \cdot 80.6 / 4.33 = 43.43$$

$$C_{inY} = \frac{4}{3} \cdot 2 \cdot 130.87 / 4.33 = 80.60$$

$$C_{inZ} = \frac{5}{3} \cdot 4 \cdot 85 / 4.33 = 130.87$$

 F) Draw a schematic diagram of the logic gates in the modified circuit indicating the actual W/L of all transistors.



G) If you inserted any inverters, calculate how much you improved the delay by doing so? Use the formula on the front page for % improvement.

$$D = N \sqrt{N+P}$$

$$\text{old: } 3(251.85)^{1/3} + 3p_{nv} + 2p_{nv} + 2p_{nv} = 25.95$$

$$\text{new: } 4(352.60)^{1/4} + 3 + 2 + 2 + 1 = 24.33$$

$$\frac{24.33 - 25.95}{25.95} = 6.23\%$$

H) Calculate how much you saved or wasted area (or energy dissipation) by doing so. You may take the total transistor widths as an indication for the area (and energy)?

$$\begin{aligned} \text{old: } & 3[\text{NAND}] + 2[\text{NOR}] + 2[\text{NAND}] + 4 \\ & = 3(1.2 \cdot 8 + 1.3) \cdot 6\mu + 2(4.8 + 1.3) \cdot 6\mu \cdot 2 \\ & \quad + 2(2.8 + 1.3) \cdot 6\mu \cdot 4 = 197.88\mu\text{m}^2 \end{aligned}$$

$$\begin{aligned} \text{new: } & 3[\text{NOT}] + 1[3\text{NOR}] + 2[\text{NAND}] + 2[\text{NOR}] + 4 \\ & = [3(2.8 + 1.3) + 3(7.5 \cdot 8 + 1.3) + 2(4.8 + 1.3) \cdot 4 \\ & \quad + 2(2.8 + 1.3) \cdot 4] \cdot 6\mu \\ & = 406.8\mu\text{m}^2 \end{aligned}$$

$$L_{\text{eff}} = .6\mu$$

$$\frac{\mu_n}{\mu_p} = \frac{8}{3}$$

$$\mu_p \propto \frac{W_p}{L_p} = \mu_n \propto \frac{W_n}{L_n}$$

$$\frac{W_p}{W_n} = \frac{8}{3} = \frac{\mu_n}{\mu_p}$$

- 5) Design a *digital modulo-6 counter* with the following characteristics:
- Three output bits: Q2,Q1,Q0
 - Synchronous count – count up on the rising edge of a clock (CLK)
 - Synchronous load – load an external input (I2,I1,I0) as the new counter state on the rising edge of CLK
 - Asynchronous clear – active-low CLEAR* signal forces the counter state to 000

The input/output signals are as follows:

CLK : active-high clock input CLEAR* :


active-low clear input

L/C* : high to select load, low to select count I2,I1,I0: parallel

data inputs

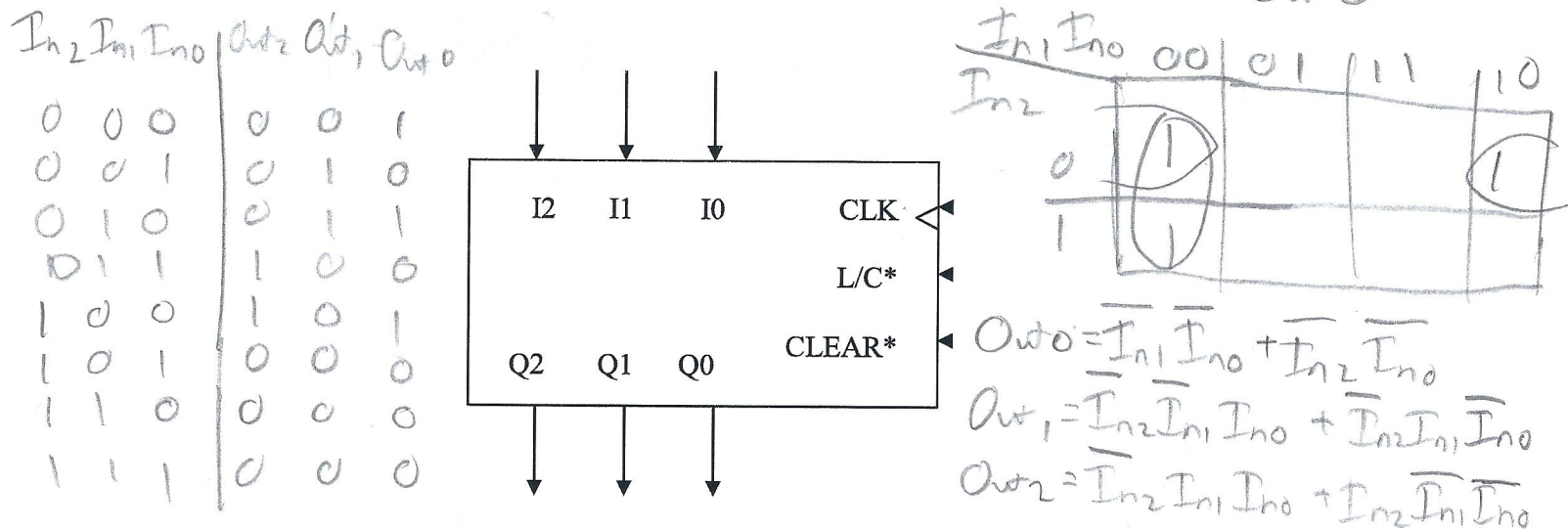Q2,Q1,Q0 : parallel data outputs

Your design must use D flip flops and simple logic gates, with the circuit minimized as much as possible. Submit your final schematic diagram and your design work.



- 9) Describe how you would test your counter design.
- What input values will you apply in each clock cycle of the test, and what output values would you expect?
 - Indicated the reason for selecting each input pattern (what aspect of the counter design is to be tested?)

